
 


- Edge-triggered J-K flip-flop

 
The **J-K flip-flop** is versatile and is a widely used type of flip-flop. The functioning of the J-K flip-flop is identical to that of the S-R flip-flop in the SET, RESET, and no-change conditions of operation. The difference is that the J-K flip-flop has no invalid state as does the S-R flip-flop.



• Edge-triggered J-K flip-flop Operation

When JK= 10

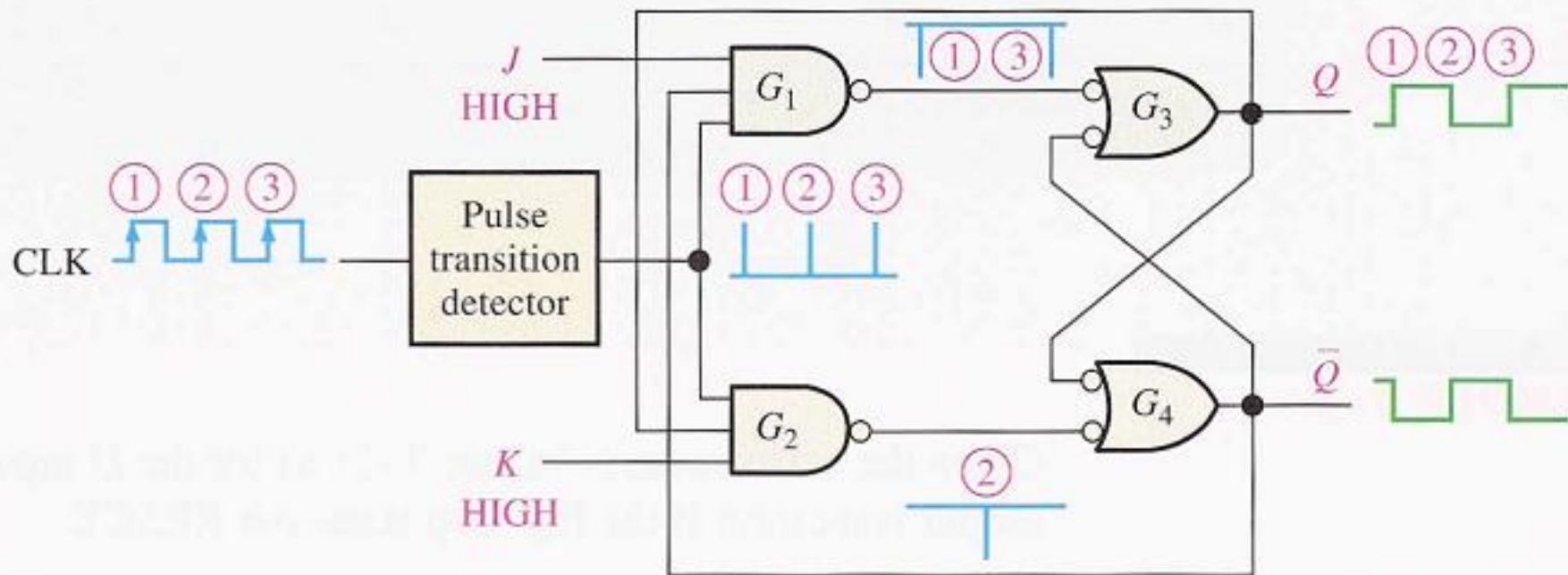
Let's assume that the flip-flop in Figure 7-23 is RESET and that the J input is HIGH and the K input is LOW rather than as shown. When a clock pulse occurs, a leading-edge spike indicated by ① is passed through gate G_1 because \bar{Q} is HIGH and J is HIGH. This will cause the latch portion of the flip-flop to change to the SET state. The flip-flop is now SET.






When JK= 00

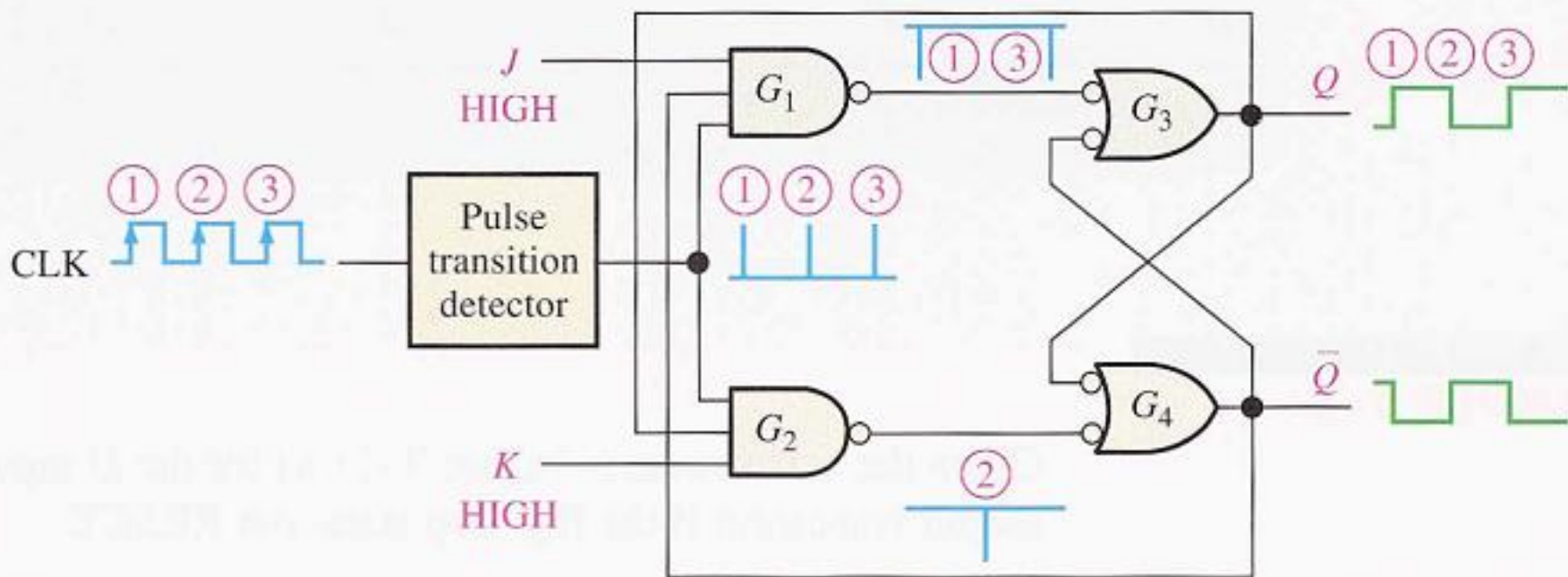If you apply a LOW to both the J and K inputs, the flip-flop will stay in its present state when a clock pulse occurs. A LOW on both J and K results in a no-change condition.




When JK= 11

So far, the logical operation of the J-K flip-flop is the same as that of the S-R type in the SET, RESET, and no-change modes. The difference in operation occurs when both the J and \bar{K} inputs are HIGH. To see this, assume that the flip-flop is RESET. The HIGH on the \bar{Q} enables gate G_1 , so the clock spike indicated by ③ passes through to set the flip-flop. Now there is a HIGH on Q , which allows the next clock spike to pass through gate G_2 and reset the flip-flop.

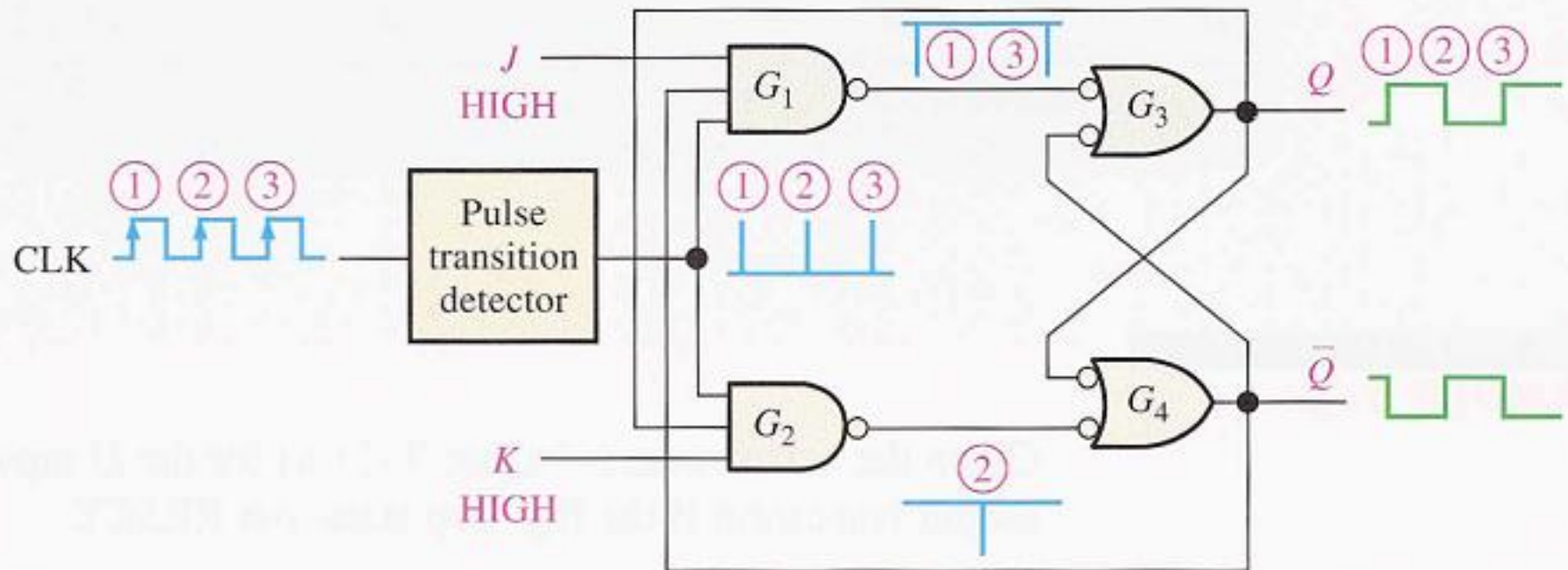

 
As you can see, on each successive clock spike, the flip-flop changes to the opposite state. This mode is called toggle operation. Figure 7-23 illustrates the transitions when the flip-flop is in the toggle mode. A J-K flip-flop connected for toggle operation is sometimes called a T flip-flop.




INPUTS			OUTPUTS		COMMENTS
J	K	CLK	Q	\bar{Q}	
0	0	\uparrow	Q_0	\bar{Q}_0	No change
0	1	\uparrow	0	1	RESET
1	0	\uparrow	1	0	SET
1	1	\uparrow	\bar{Q}_0	Q_0	Toggle



\uparrow = clock transition LOW to HIGH

 Q_0 = output level prior to clock transition




INPUTS			OUTPUTS		COMMENTS
J	K	CLK	Q	\bar{Q}	
0	0	\uparrow	Q_0	\bar{Q}_0	No change
0	1	\uparrow	0	1	RESET
1	0	\uparrow	1	0	SET
1	1	\uparrow	\bar{Q}_0	Q_0	Toggle

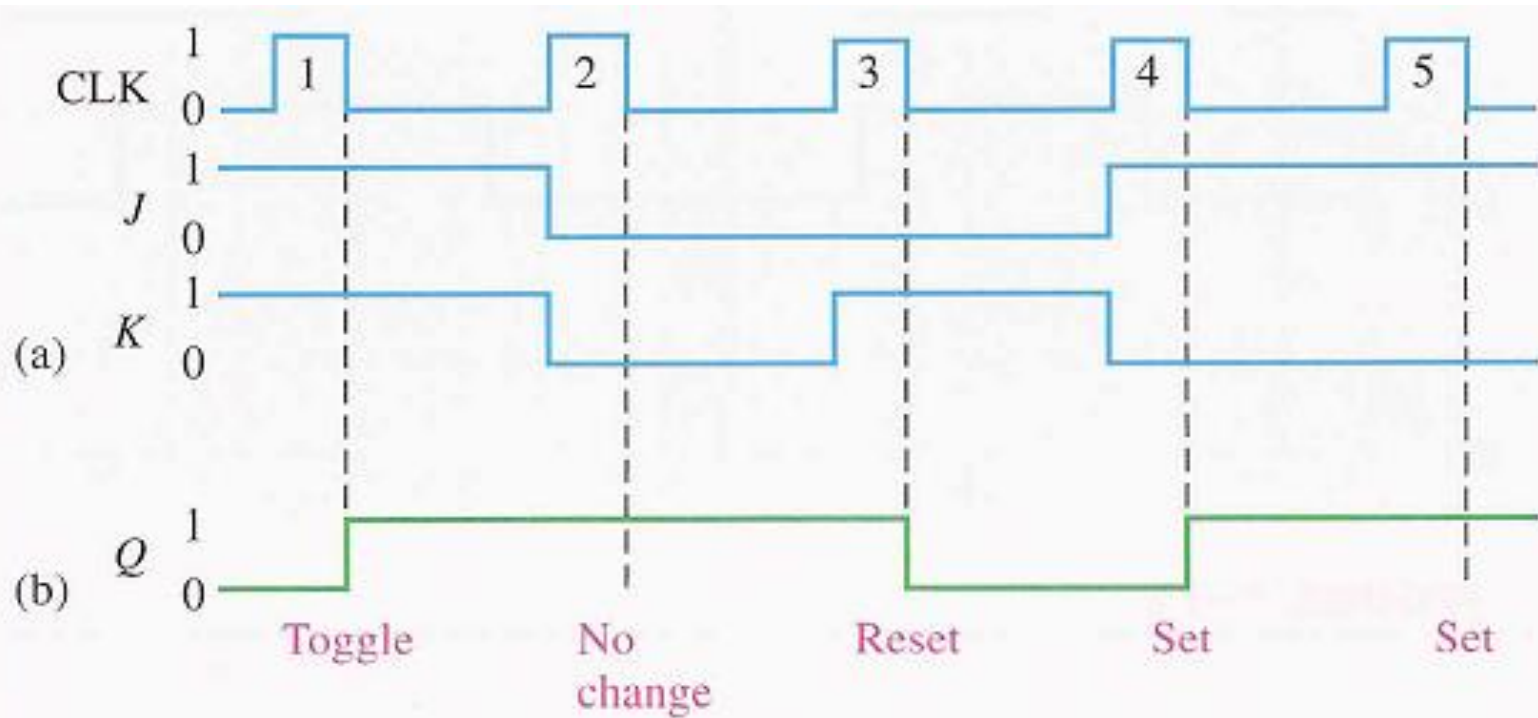

  

T flip-flop

 A T flip-flop can only maintain or complement its current state.



C	T	Q_{next}
0	x	No change
1	0	No change
1	1	Q'_{current}

Characteristic tables

- The tables that we've made so far are called **characteristic tables**.
 - They show the next state $Q(t+1)$ in terms of the current state $Q(t)$ and the inputs.
 - For simplicity, the control input C is usually not listed.
 - Again, these tables don't indicate the positive edge-triggered nature of the flip-flops.

D	$Q(t+1)$	Operation
0	0	Reset
1	1	Set

J	K	$Q(t+1)$	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T	$Q(t+1)$	Operation
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Characteristic equations

- We can also write **characteristic equations**, where the next state $Q(t+1)$ is defined in terms of the current state $Q(t)$ and the flip-flop inputs.

D	$Q(t+1)$	Operation
0	0	Reset
1	1	Set

$$Q(t+1) = D$$

J	K	$Q(t+1)$	Operation
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement


$$Q(t+1) = K'Q(t) + JQ'(t)$$

T	$Q(t+1)$	Operation
0	$Q(t)$	No change
1	$Q'(t)$	Complement

$$\begin{aligned} Q(t+1) &= T'Q(t) + TQ'(t) \\ &= T \oplus Q(t) \end{aligned}$$

Flip-flop review

Flip-flops

 


Characteristic tables

D	Q(t+1)	Operation
0	0	Reset
1	1	Set


Characteristic equations

$$Q(t+1) = D$$

 

J	K	Q(t+1)	Operation
0	0	Q(t)	No change
0	1	0	Reset
1	0	1	Set
1	1	Q'(t)	Complement

$$Q(t+1) = K'Q(t) + JQ'(t)$$


 


T	Q(t+1)	Operation
0	Q(t)	No change
1	Q'(t)	Complement

$$Q(t+1) = T \oplus Q(t)$$



Master-Slave Flip Flop

  A Master-Slave Flip-flop is constructed from two separate flip-flops. One circuit serves as a Master and the other as a Slave.





The Master-Slave JK Flip-flop

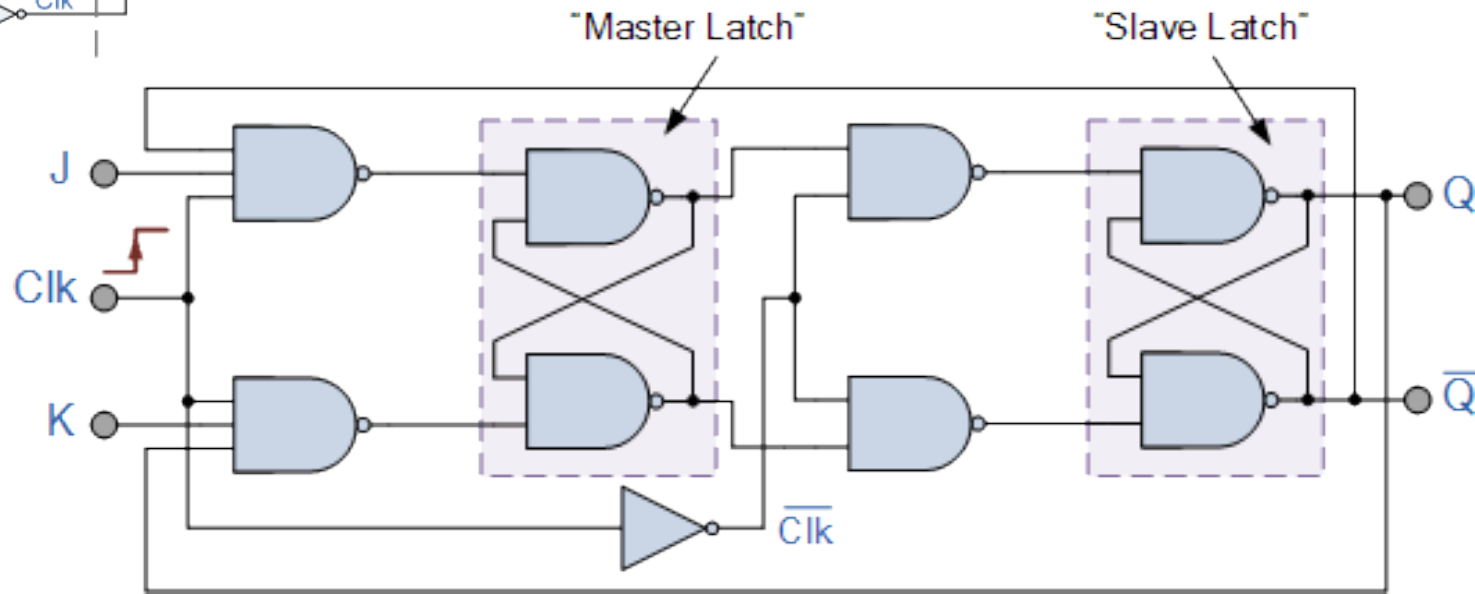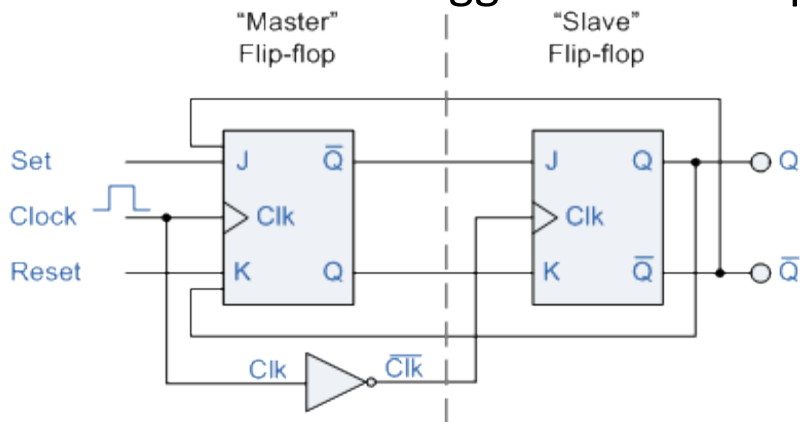- The outputs from Q and \bar{Q} from the "Slave" flip-flop are fed back to the inputs of the "Master" with the outputs of the "Master" flip-flop being connected to the two inputs of the "Slave" flip-flop. This feedback configuration from the slave's output to the master's input gives the characteristic toggle of the JK flip-flop as shown below.



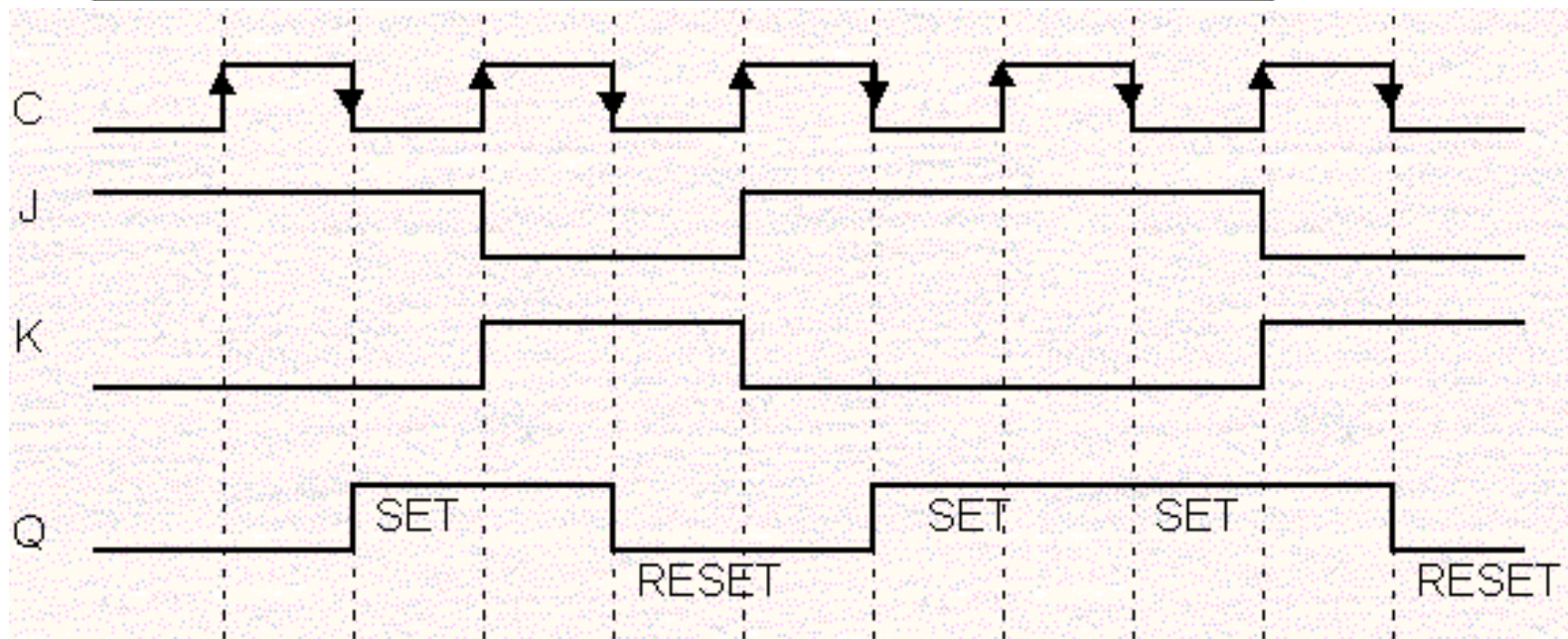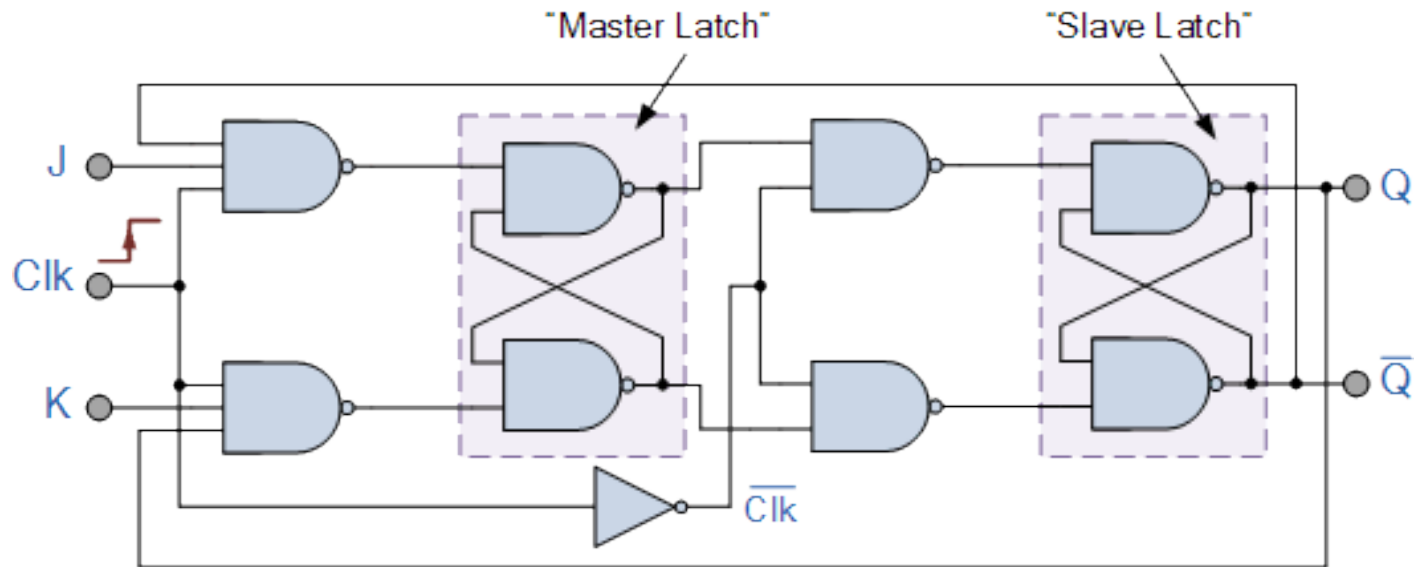
The circuit accepts the value in the input when the clock is HIGH, and passes the data to the output on the falling-edge of the clock signal.



Asynchronous Preset and Clear Inputs


For the flip-flops just discussed, the S - R , D , and J - K inputs are called *synchronous inputs* because data on these inputs are transferred to the flip-flop's output only on the triggering edge of the clock pulse; that is, the data are transferred synchronously with the clock.

Most integrated circuit flip-flops also have **asynchronous** inputs. These are inputs that affect the state of the flip-flop *independent of the clock*. They are normally labeled **preset** (\overline{PRE}) and **clear** (\overline{CLR}), or *direct set* (S_D) and *direct reset* (R_D) by some manufacturers. An active level on the preset input will set the flip-flop, and an active level on the clear input will reset it.

 

\overline{PRE}	\overline{CLR}	FF response
1	1	Clocked operation*
0	1	$Q = 1$ (regardless of CLK)
1	0	$Q = 0$ (regardless of CLK)
0	0	Not used



*Q will respond to J, K, and CLK

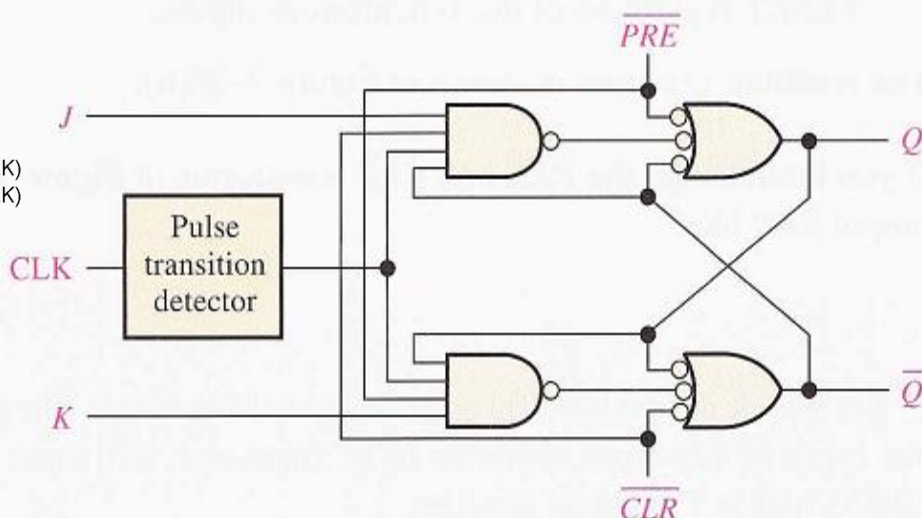

puts work. As you can see, they are connected so that they override the effect of the synchronous inputs, J , K , and the clock.

  EXAMPLE 7-8

For the positive edge-triggered J-K flip-flop with preset and clear inputs in Figure 7-28, determine the Q output for the inputs shown in the timing diagram in part (a) if Q is initially LOW.



1. During clock pulses 1, 2, and 3, the preset (\overline{PRE}) is LOW, keeping the flip-flop SET regardless of the synchronous J and K inputs.
2. For clock pulses 4, 5, 6, and 7, toggle operation occurs because J is HIGH, K is HIGH, and both \overline{PRE} and \overline{CLR} are HIGH.
3. For clock pulses 8 and 9, the clear (\overline{CLR}) input is LOW, keeping the flip-flop RESET regardless of the synchronous inputs.



FLIP-FLOP APPLICATIONS

three general applications of flip-flops are


Parallel Data Storage

Frequency Division



Counting

Parallel Data Storage

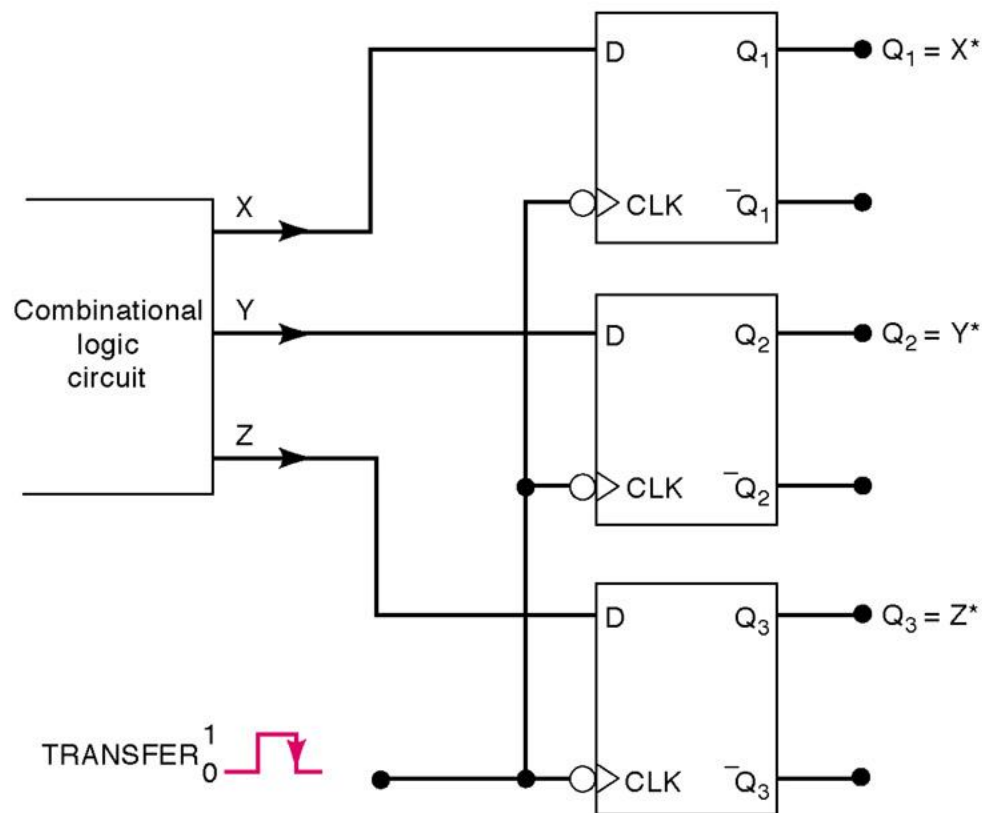- Flip flops store outputs from combinational logic.
- Multiple flops can store a collection of data





*After occurrence of NGT

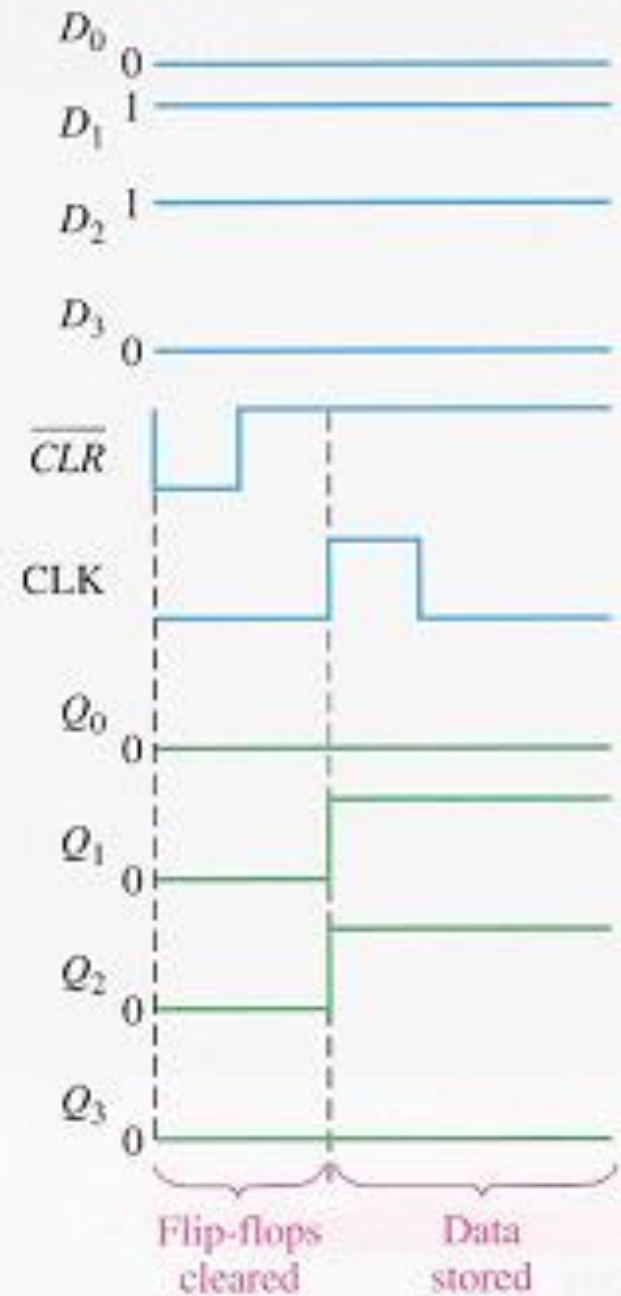
 


Frequency Division

Another application of a flip-flop is dividing (reducing) the frequency of a periodic waveform. When a pulse waveform is applied to the clock input of a J-K flip-flop that is connected to toggle ($J = K = 1$), the Q output is a square wave with one-half the frequency of the clock input. Thus, a single flip-flop can be applied as a divide-by-2 device, as is illustrated in Figure 7-37. As you can see, the flip-flop changes state on each triggering clock edge (positive edge-triggered in this case). This results in an output that changes at half the frequency of the clock waveform.

  

  Further division of a clock frequency can be achieved by using the output of one flip-flop as the clock input to a second flip-flop, as shown in Figure 7–38. The frequency of the Q_A output is divided by 2 by flip-flop B. The Q_B output is, therefore, one-fourth the frequency of the original clock input. Propagation delay times are not shown on the timing diagrams.





By connecting flip-flops in this way, a frequency division of 2^n is achieved, where n is the number of flip-flops. For example, three flip-flops divide the clock frequency by $2^3 = 8$; four flip-flops divide the clock frequency by $2^4 = 16$; and so on.



Counting



Another important application of flip-flops is in digital counters

Both flip-flops are initially RESET. Flip-flop A toggles on the negative-going transition of each clock pulse. The Q output of flip-flop A clocks flip-flop B, so each time Q_A makes a HIGH-to-LOW transition, flip-flop B toggles. The resulting Q_A and Q_B waveforms are shown in the figure.

 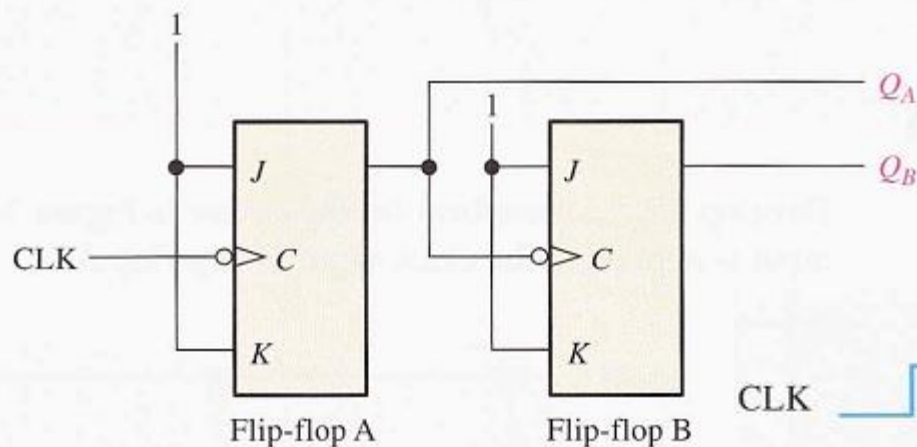

  EXAMPLE 7-11

Determine the output waveforms in relation to the clock for Q_A , Q_B , and Q_C in the circuit of Figure 7-42 and show the binary sequence represented by these waveforms.




FLIP-FLOP OPERATING CHARACTERISTICS

The performance, operating requirements, and limitations of flip-flops are specified by several operating characteristics or parameters found on the data sheet for the device. Generally, the specifications are applicable to all CMOS and TTL flip-flops.

Propagation Delay Times


A **propagation delay time** is the interval of time required after an input signal has been applied for the resulting output change to occur. Four categories of propagation delay times are important in the operation of a flip-flop.

 1. Propagation delay t_{PLH} as measured from the triggering edge of the clock pulse to the LOW-to-HIGH transition of the output. This delay is illustrated in Figure 7-32(a).



(a)

 
2. Propagation delay t_{PHL} as measured from the triggering edge of the clock pulse to the HIGH-to-LOW transition of the output. This delay is illustrated in Figure 7–32(b).



 3. Propagation delay t_{PLH} as measured from the leading edge of the preset input to the LOW-to-HIGH transition of the output. This delay is illustrated in Figure 7–33(a) for an active-LOW preset input.
4. Propagation delay t_{PHL} as measured from the leading edge of the clear input to the HIGH-to-LOW transition of the output. This delay is illustrated in Figure 7–33(b) for an active-LOW clear input.


Set-up Time

The **set-up time** (t_s) is the minimum interval required for the logic levels to be maintained constantly on the inputs (J and K , or S and R , or D) prior to the triggering edge of the clock pulse in order for the levels to be reliably clocked into the flip-flop. This interval is illustrated in Figure 7–34 for a D flip-flop.



Hold Time

 The **hold time** (t_h) is the minimum interval required for the logic levels to remain on the inputs after the triggering edge of the clock pulse in order for the levels to be reliably clocked into the flip-flop. This is illustrated in Figure 7-35 for a D flip-flop.



Maximum Clock Frequency

The maximum clock frequency (f_{\max}) is the highest rate at which a flip-flop can be reliably triggered. At clock frequencies above the maximum, the flip-flop would be unable to respond quickly enough, and its operation would be impaired.

Pulse Widths

Minimum pulse widths (t_w) for reliable operation are usually specified by the manufacturer for the clock, preset, and clear inputs. Typically, the clock is specified by its minimum HIGH time and its minimum LOW time.

Power Dissipation

The **power dissipation** of any digital circuit is the total power consumption of the device. For example, if the flip-flop operates on a +5 V dc source and draws 5 mA of current, the power dissipation is

$$P = V_{CC} \times I_{CC} = 5 \text{ V} \times 5 \text{ mA} = 25 \text{ mW}$$

Comparison of Specific Flip-Flops

PARAMETER	CMOS		TTL	
	74HC74A	74AHC74	74LS74A	74F74
t_{PHL} (CLK to Q)	17 ns	4.6 ns	40 ns	6.8 ns
t_{PLH} (CLK to Q)	17 ns	4.6 ns	25 ns	8.0 ns
t_{PHL} (\overline{CLR} to Q)	18 ns	4.8 ns	40 ns	9.0 ns
t_{PLH} (\overline{PRE} to Q)	18 ns	4.8 ns	25 ns	6.1 ns
t_s (set-up time)	14 ns	5.0 ns	20 ns	2.0 ns
t_h (hold time)	3.0 ns	0.5 ns	5 ns	1.0 ns
t_W (CLK HIGH)	10 ns	5.0 ns	25 ns	4.0 ns
t_W (CLK LOW)	10 ns	5.0 ns	25 ns	5.0 ns
t_W ($\overline{CLR}/\overline{PRE}$)	10 ns	5.0 ns	25 ns	4.0 ns
f_{max}	35 MHz	170 MHz	25 MHz	100 MHz
Power, quiescent	0.012 mW	1.1 mW		
Power, 50% duty cycle			44 mW	88 mW



Reference:

**Mixed contents from books by Floyd; Mano; Vahid
And Howard.**

Acknowledgement:

Nafiz Ahmed Chisty



Thanks